

U.S.N.

--	--	--	--	--	--	--	--	--	--

BMS College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

October / November 2021 Supplementary Examinations

Programme: B.E.

Branch: ALL

Course Code: 14EC1ICEEE / 14EC2ICEEE

Course: ELEMENTS OF ELECTRONICS ENGINEERING

Semester: I / II

Duration: 3 hrs.

Max Marks: 100

Date: 30.10.2021


Instructions: Answer Any FIVE FULL questions choosing one from each unit.

UNIT 1

- 1
 - a For the voltage divider bias circuit, determine I_B , I_C , V_{CE} , V_C , V_E , V_B . Supply voltage is 20V and resistor values are $R_1=18.6K\Omega$, $R_2=11.4K\Omega$, $R_C=1 K\Omega$ and $R_E=1 K\Omega$. Assume transistor with $\beta=50$. 10
 - b Classify FET and draw their symbols. 04
 - c Distinguish between BJT and FET. 06

OR

- 2
 - a With neat schematic, explain the working principle of N-channel depletion type MOSFET 10
 - b Identify the following V-I characteristics and comment on operation of circuit used to get same. 10

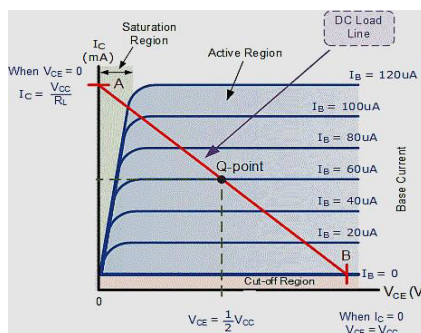

UNIT 2


- 3
 - a Classify amplifiers based on different criteria with a brief description. 10
 - b Explain the working of BJT as a linear amplifier. 10

OR

- 4 a Compare CE, CB and CC transistor configuration and identify one application where they can be used. Draw each configuration **10**
 b Analyze the impact of feedback on different feedback topologies. **10**


UNIT 3

- 5 a Draw the circuit diagram of Hartley oscillator and explain its operation. **08**
 b Derive the expression for output voltage of an Op-Amp differentiator **08**
 c For the following Op-amp circuit, $R_g = 12K\Omega$ and gain $A = 50$. Determine the value of feedback resistance. ($V_{CC} = 12V$ and $-V_{EE} = -12V$). **04**

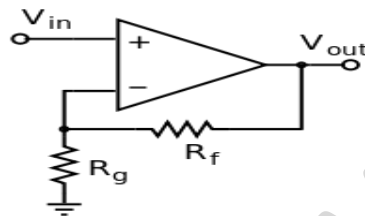

UNIT 4

- 6 a Explain the switching circuit operation of NAND and NOR Gates **05**
 b Perform the following **05**
 $(1A0.65)_{16} = ()_2 = ()_{10} = ()_8$
 c Perform Binary Subtraction using 1's complement method and verify the same using 2's complement. **05**
 $(101101-111010)_2$
 d Analyze the logic circuit shown in fig. Determine the Boolean function for y and state its truth table. **05**

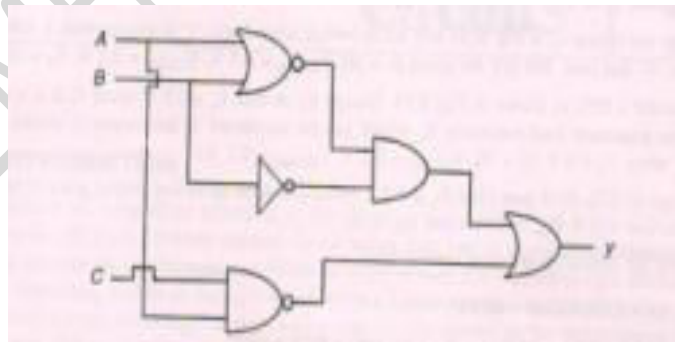

UNIT 5

- 7 a Explain about seven segment display and mention its applications. **07**
 b What is IOT? explain the concept through a block diagram **07**
 c Explain the evolution of cellular communication. **06**
