

# B. M. S. College of Engineering, Bengaluru - 560019

Autonomous Institute Affiliated to VTU  
October / November 2021 Supplementary Examinations

Programme: B.E.

Branch : ALL

Course Code: 18EC1ESECE / 18EC2ESECE

Course: Elements of Electronics Engineering

Semester : I / II

Duration: 3 hrs.

Max Marks: 100

Date: 30.10.2021

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may suitably assumed.

## UNIT - I

1. a) What is PN junction? With the help of neat diagrams, explain the VI characteristics of PN junction diode. **08**
- b) A bridge rectifier supplies a load of  $10K\Omega$ . The ac voltage applied to the diode is  $6V V_{rms}$ . If the diode forward resistance is neglected, calculate  $i_{dc}$ , output current. ii) dc output voltage. iii) ripple factor. **06**
- c) With a neat circuit diagram, explain the working of Zener diode voltage regulator. **06**

## UNIT - II

2. a) With a neat circuit diagram and input output characteristics, explain the working of NPN transistor CE configuration. **08**
- b) With a neat diagram, explain the working of transistor as a switch. **06**
- c) An amplifier has an input signal of  $0.5V$  and draws  $1.5mA$  from the source. It delivers  $10V$  to a load at  $15mA$  find. i) voltage gain ii) current gain iii) power gain. **06**


## OR

3. a) Derive the expression for  $V_{CE}$  and  $I_E$  of a voltage divider bias circuit. **08**
- b) With a neat block diagram, derive the expression for feedback gain of an negative feedback system. **06**
- c) What are the advantages of negative feedback amplifier? Explain any one in detail. **06**

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

### UNIT - III

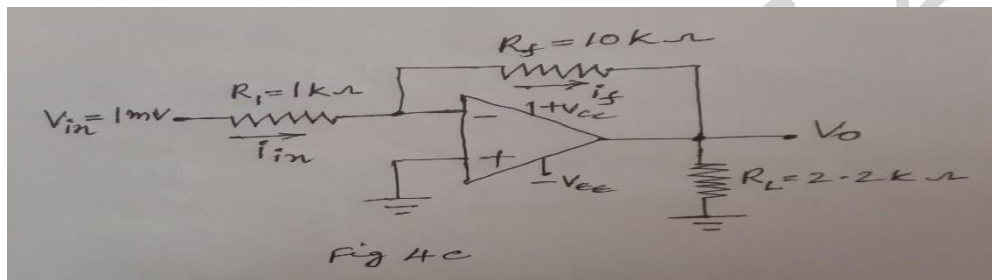4. a) With a neat circuit diagram, explain the working of Colpitts oscillator. **08**
- b) Derive the expression for output voltage of a three input Non-inverting summing amplifier using Op-Amp. **06**
- c) For the inverting amplifier shown in fig 4C, determine  $A_f$ ,  $V_o$ ,  $i_{in}$ ,  $i_f$ , and  $i_L$ . **06**



### UNIT - IV

5. a) Realize EX-NOR gate using basic gates and NOR gates. **06**
- b) Convert the given expression in standard POS form: **06**  
 $f(a, b, c) = (a + b)(b + c')(a + c)$
- c) Simplify the given expression and implement using NAND gates and basic gates:  $F = (w x + w y')(x + w) + w x(x' + y')$  **08**

**OR**

6. a) Simplify the given expression using 3-variable K-map: **04**  
 $f(a, b, c) = \sum (1, 2, 3, 6, 7)$
- b) What is multiplexer? With a neat logic diagram and truth table, explain the working of 8:1 multiplexer. **08**
- c) What is a decoder? Implement 3X8 decoder. **08**

### UNIT - V

7. a) List the difference between analog and digital signals. **03**

- b) With a neat block diagram, explain the working of digital communication system. **10**
- c) Discuss the evolution of cellular communication system. **07**

\*\*\*\*\*

SUPPLEMENTARY EXAMS 2021